
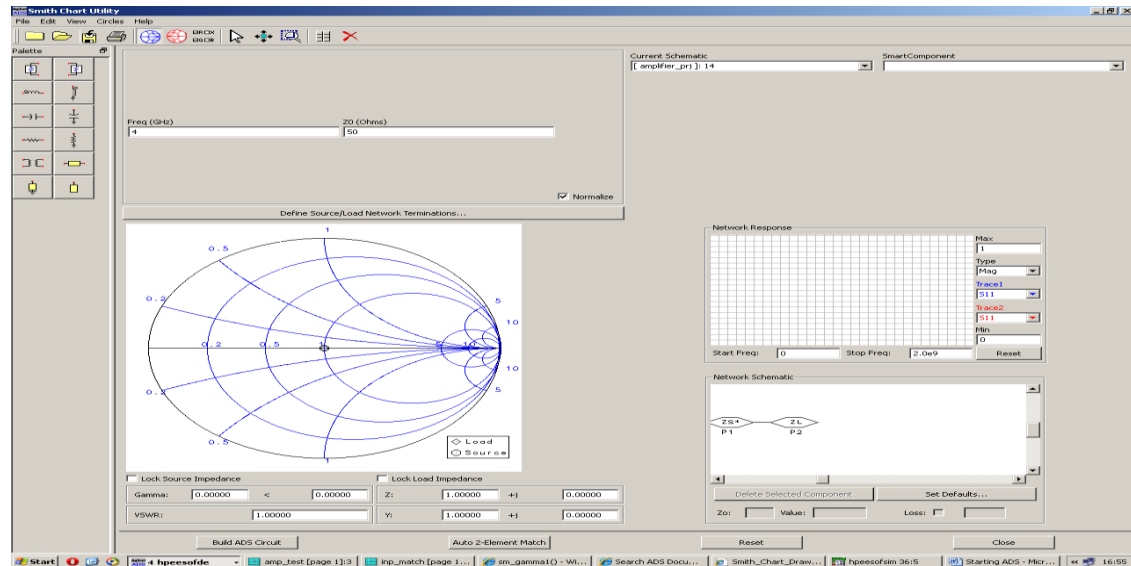


Starting Smith Chart Utility:

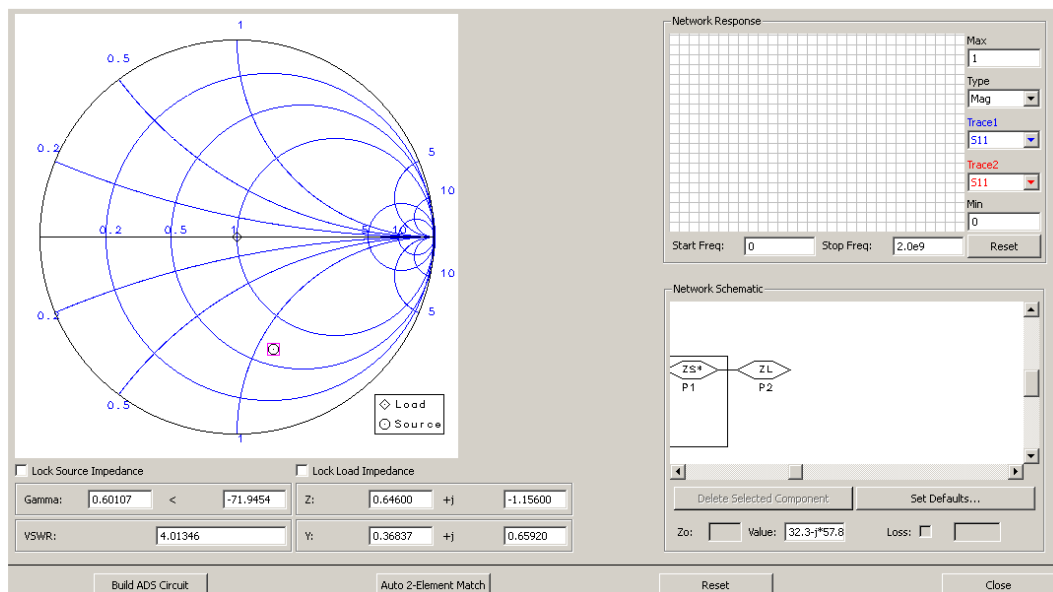
- Find the **Smith Chart** in the **Tools** in **Schematic** and you will see window as shown below:



- Set the frequency and insert the Γ_s (SmGamma1) or Γ_L (SmGamma2) and lock the load and source impedance by ticking the box.



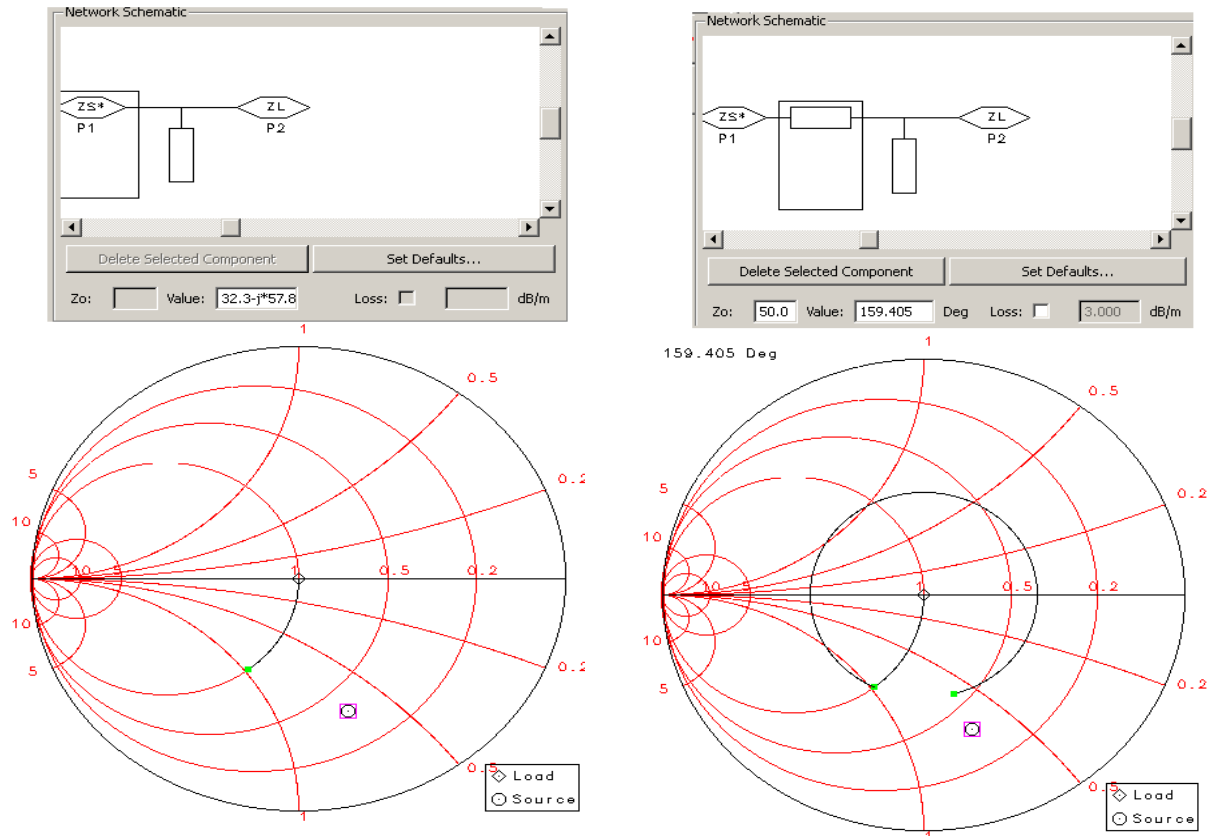- Starting from the load, choose the required transmission line component for each input or output matching circuit. Since we are calculating in admittance, activate the admittance chart icon (red chart).



- Adjust the electrical length or impedance values for each of the transmission line component in your input or output matching circuit to reach the intended Γ_s or Γ_L as shown below.

